

# ECE 230L - LAB 7

## DEVICE NON-IDEALITIES

### Contents

<b>1</b>	<b>Objectives of this Laboratory</b>	<b>2</b>
<b>2</b>	<b>Experimental Exploration Format</b>	<b>2</b>
<b>3</b>	<b>Experimental Explorations</b>	<b>3</b>
3.1	Thermal Effects on PN-Junction Diode & MOSFET . . . . .	3
3.2	MOSFET Amplifier Gain and Load Limits . . . . .	5
3.3	MOSFET Input and Output Resistance . . . . .	6
3.4	MOSFET Inverter maximum clock frequency with external capacitive load . . . .	6
3.5	Zener diode (Reverse breakdown) . . . . .	6
	<b>Grading Rubric</b>	<b>7</b>

### List of Figures

1	PN-Junction Diode Test Circuit . . . . .	3
2	Circuit used to characterize an NMOSFET . . . . .	4

## 1 Objectives of this Laboratory

The objectives of this laboratory session are as follows:

- To gain understanding of some of the less than ideal behavior of devices and circuits explored in previous laboratories.
- To explore methods for measuring these non-idealities in a less structured lab environment using the tools presented during the course of the semester.
- To work with a group in the course to explore these methods.
- To present group findings to fellow students in the course in a lab presentation.

## 2 Experimental Exploration Format

- This lab will be conducted in groups of two or three.
- Each group will be assigned an exploration
- Complete the exploration and form a brief presentation to share with the lab section—you *have one hour*
- Each group will present their findings to the entire lab

### 3 Experimental Explorations

There are five possible explorations:

#### 3.1 Thermal Effects on PN-Junction Diode & MOSFET

*To be completed in a group of 2 or 3.*

##### PN-Junction Diode

1. Construct the following circuit on a breadboard:


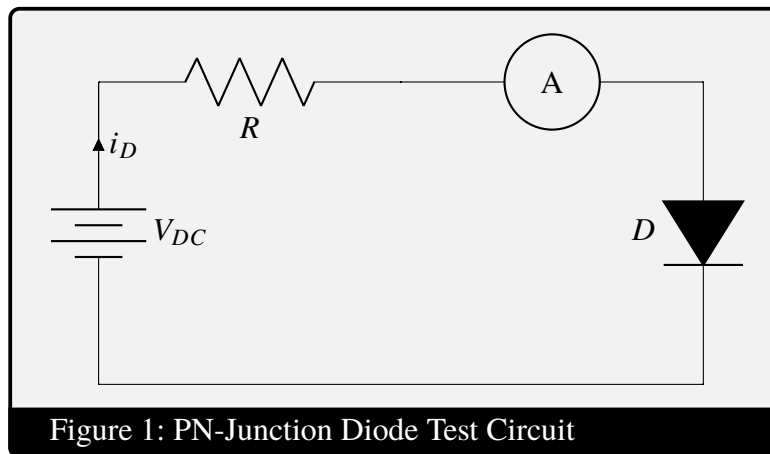
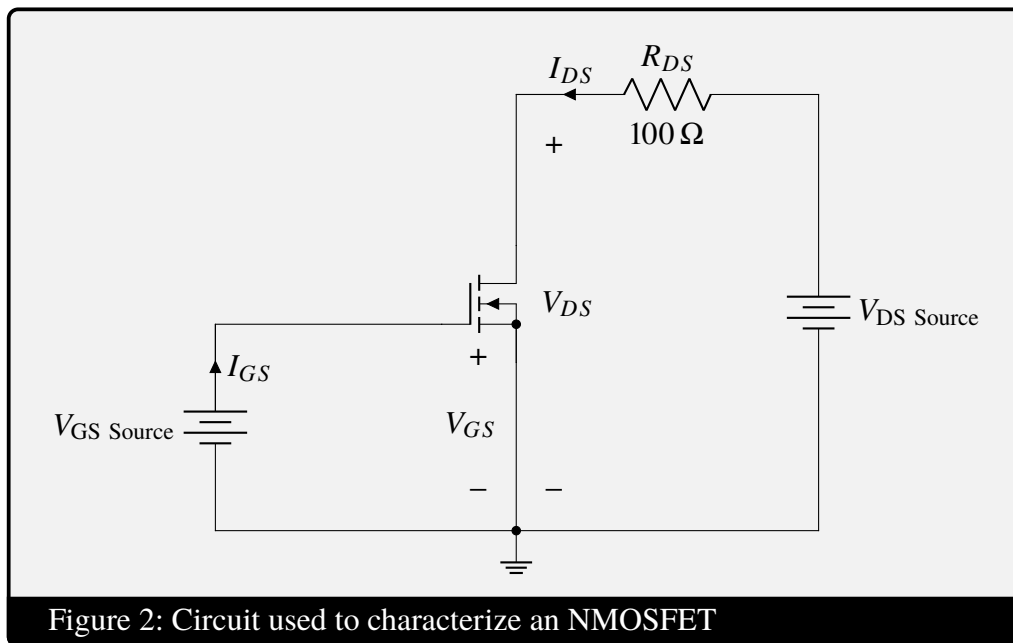
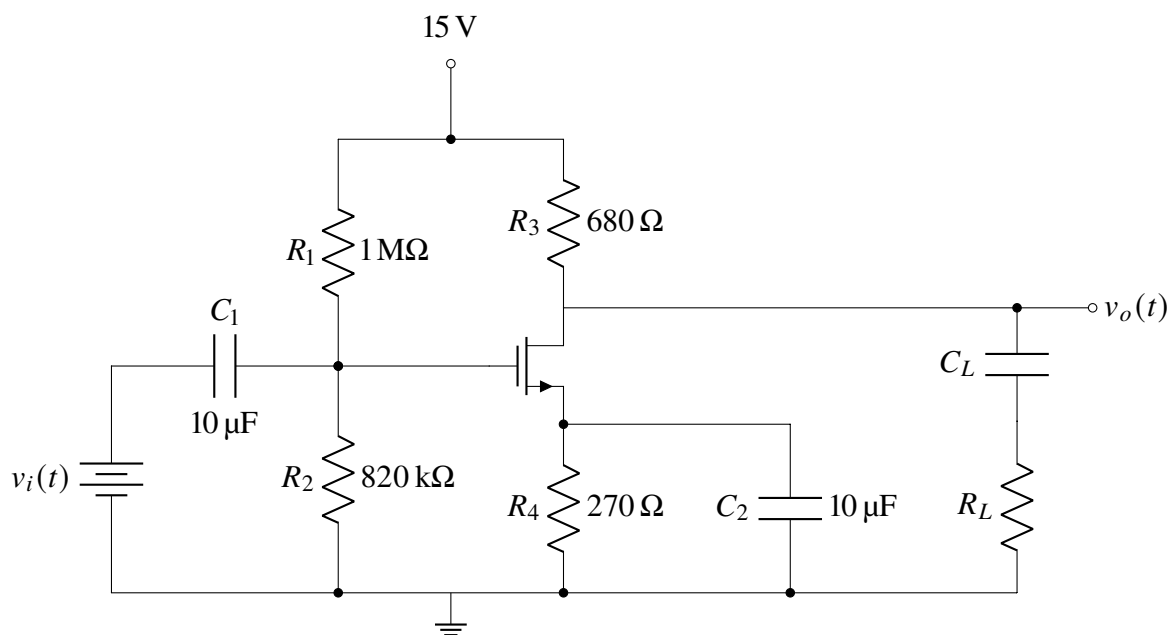



Figure 1: PN-Junction Diode Test Circuit

2. Run the `singleloop.vi` script from 0 to 6 V with 100 steps. This produces  $I_D(V_D)$ .
3. Repeat the above, but with a voltmeter over the diode, to measure  $V_{PN}$ . Combine the results to produce the graph  $I_D(V_{PN})$ .
4. Now, obtain thermal paste from your TA and apply it to the diode. Obtain a soldering iron and heat it to its lowest setting. Apply the soldering iron to the diode to allow it to heat it.
5. Repeat steps (1) – (3), and compare the results.

**MOSFET**
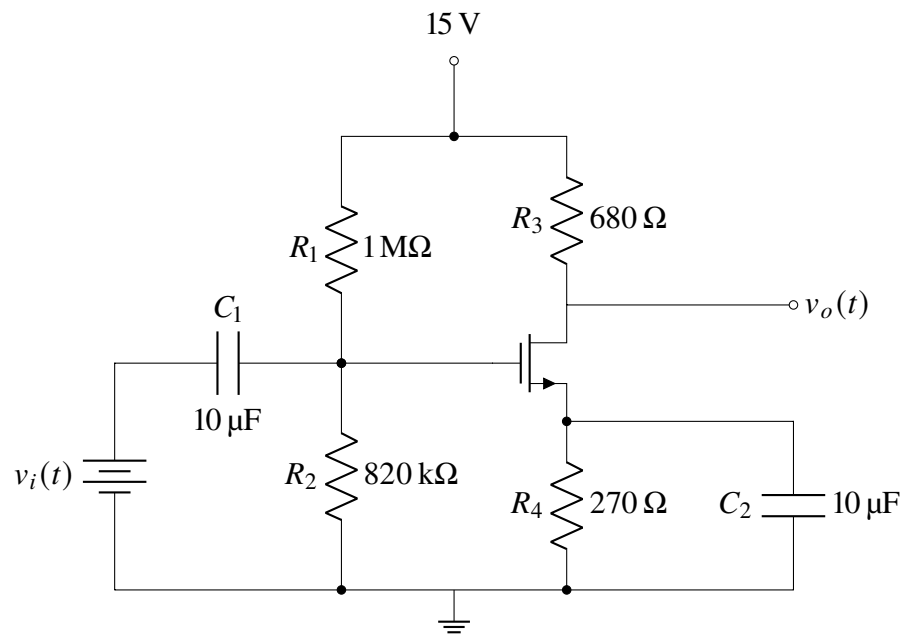
### 3.2 MOSFET Amplifier Gain and Load Limits



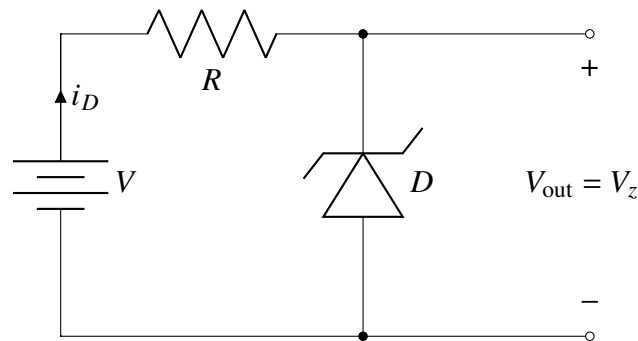**3.3 MOSFET Input and Output Resistance****3.4 MOSFET Inverter maximum clock frequency with external capacitive load****3.5 Zener diode (Reverse breakdown)**

## Grading Rubric