

Table 1: ECE 230L Laboratory 3 Grading Rubric

Criteria	Points Possible
DC Analysis	10
Circuit Diagram	5
Waveforms	5
AC Analysis	10
Circuit Diagram	5
Waveforms	5
Transient Analysis	10
Circuit Diagram	5
Waveforms	5
Practice Exercise	35
Circuit Diagram	5
DC Analysis	10
AC Analysis	10
Transient Analysis	10
Thévenin Equivalent Example Circuit	20
Circuit Diagram	10
V_{OC} and I_{SC} Labeled	5
Correct R_{TH} Value	5
Thévenin Equivalent Challenge Circuit	15
Circuit Diagram	5
V_{OC} and I_{SC} Labeled	5
Correct R_{TH} Value	5
Total	100